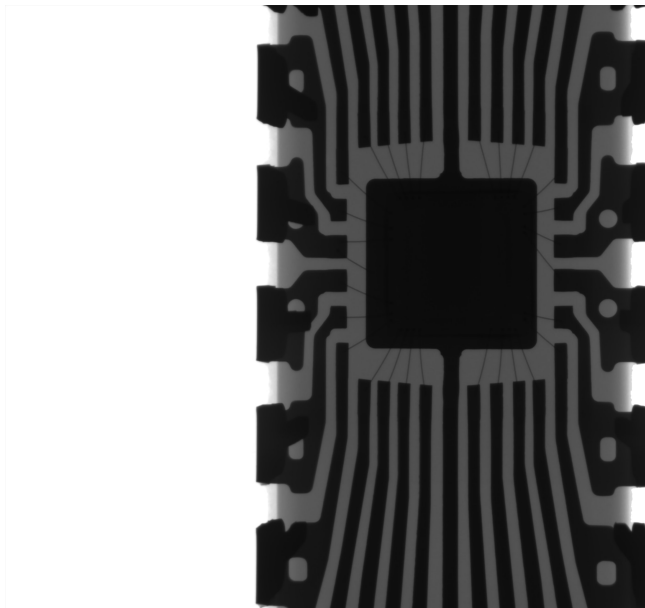


# Electric Circuits Exercises



GitHub: <https://github.com/klaidis>


Last Update on: 27/05/2021

Indice

<b>1</b>	<b>DC CIRCUIT</b>	<b>1</b>
1.1	DC-01 . . . . .	1
1.2	DC-02 . . . . .	1
1.3	DC-03 . . . . .	2
1.4	DC-04 . . . . .	3
1.5	DC-05 . . . . .	3
1.6	DC-06 . . . . .	4
1.7	DC-07 . . . . .	5
1.8	DC-08 . . . . .	5
1.9	DC-09 . . . . .	6
<b>2</b>	<b>AC CIRCUIT</b>	<b>7</b>
2.1	AC-01 . . . . .	7
2.2	AC-02 . . . . .	7
2.3	AC-03 . . . . .	8
2.4	AC-04 . . . . .	9

# 1 DC CIRCUIT

## 1.1 DC-01

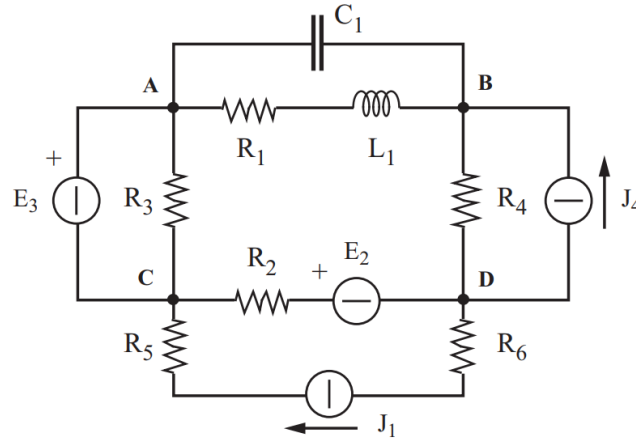


$$\begin{array}{llll} R_1 = 2 \, \Omega & R_2 = 2 \, \Omega & R_3 = 5 \, \Omega & R_4 = 1 \, \Omega \\ R_5 = 2 \, \Omega & R_6 = 1 \, \Omega & C_1 = 200 \, \mu F & L_1 = 10 \, mH \\ E_3 = 40 \, V & J_1 = 20 \, A & J_4 = 5 \, A & P_{R2} = 0 \, W \end{array}$$

Solution:

$$\begin{array}{l} I_{R3}=8 \, A, I_{E3}=28 \, A, I_{R4}=25 \, A, U_{J4}=25 \, V \\ I_{R1}=20 \, A, U_{C1}=40 \, V, E_2=25 \, V, U_{J1}=85 \, V \\ P_{R3}=320 \, W, P_{R4}=625 \, W, P_{E3}=1120 \, W, P_{J4}=125 \, W \\ W_{C1}=0.16 \, J, W_{L1}=2 \, J, P_{J1}=1700 \, W \end{array}$$

## 1.2 DC-02

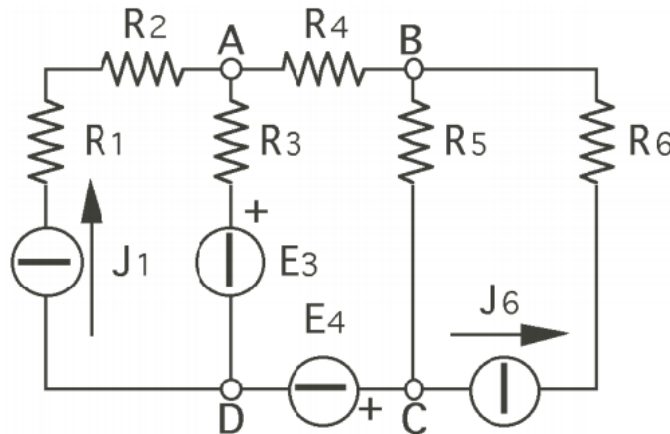


$$\begin{array}{lllll} R_1 = 1.5 \, \Omega & R_2 = 2.5 \, \Omega & R_3 = 4 \, \Omega & R_4 = 5 \, \Omega & R_5 = 8 \, \Omega \\ R_6 = 3.5 \, \Omega & J_1 = 5 \, A & E_3 = 100 \, V & E_4 = 50 \, V & P_{J1} = 100 \, W \end{array}$$

Solution:

$$\begin{array}{l} U_{J1} = 20 \, V, U_{AD} = 0 \, V, J_6 = -55 \, A, U_{J6} = -392.5 \, V, P_{R3} = 2500 \, W \\ I_{E4} = -30 \, A, P_{R4} = 4500 \, W, P_{J6} = 21587.5 \, W, U_{BC} = -200 \, V \end{array}$$

### 1.3 DC-03

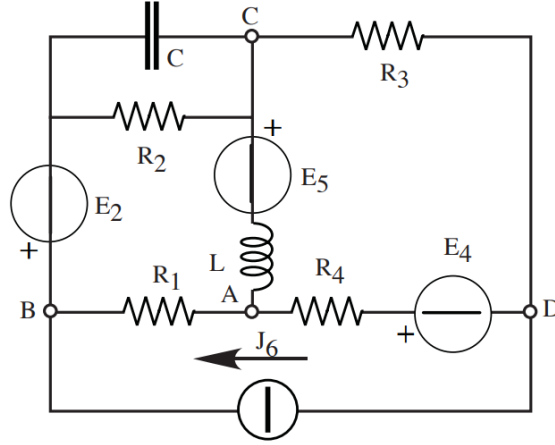

$$\begin{array}{lllll} R_1 = 20 \, \Omega & R_2 = 40 \, \Omega & R_3 = 50 \, \Omega & R_4 = 20 \, \Omega & L = 10 \, mH \\ C = 20 \, \mu F & E_2 = -900 \, V & E_4 = 100 \, V & E_5 = 800 \, V & J_6 = 25 \, A \end{array}$$

Assuming  $V_A = 0$ , **determine**:

- $V_B, V_C, V_D$  potentials.
- The values of the stored energies  $W_L$  and  $W_C$  respectively from the inductor and capacitor.
- The value of the power  $P_{R_3}$  absorbed by resistor  $R_3$ .

Solution:

$$J_2 = \frac{E_2}{R_2} = -22,5 \, A \quad G_2 = \frac{1}{R_2} = 1/40 \, S$$

$$J_4 = \frac{E_4}{R_4} = 5 \, A \quad G_4 = \frac{1}{R_4} = 1/20 \, S$$

$$\begin{cases} J_6 + J_2 = V_B (G_1 + G_2) - V_C G_2 \\ I_{E_5} - J_2 = -V_B G_2 + V_C (G_2 + G_3) - V_D G_3 \\ -J_4 - J_2 = -V_C G_3 + V_D (G_3 + G_4) \\ V_C - V_A = E_5 \end{cases}$$

$$\begin{cases} V_B = \frac{J_2 + J_6 + E_5 G_2}{G_1 + G_2} = 300 \, V \\ V_C = E_5 = 800 \, V \\ V_D = \frac{-J_4 - J_6 + E_5 G_3}{G_3 + G_4} = -200 \, V \\ I_{E_5} = J_2 - V_B G_2 + V_C (G_2 + G_3) - V_D G_3 = 10 \, A \end{cases}$$


$$U_C = E_2 + (V_C - V_B) = -400 \, V$$

$$W_C = \frac{1}{2} C U_C^2 = 1,6 \, J$$

$$W_L = \frac{1}{2} L I_L^2 = \frac{1}{2} L I_{E_5}^2 = 0,5 \, J$$

$$P_{R_3} = (V_C - V_D)^2 G_3 = 20 \, kW$$

## 1.4 DC-04

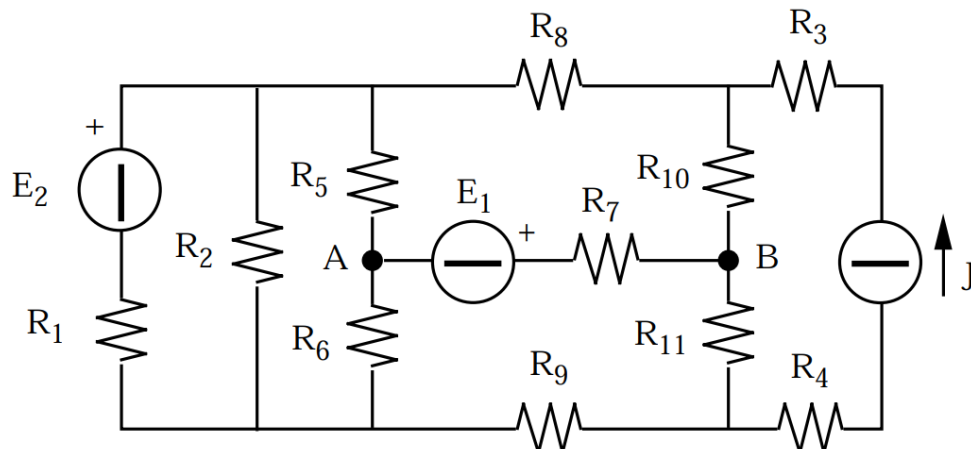

$$\begin{array}{lllll}
 R_1 = 60 \, \Omega & R_2 = 60 \, \Omega & R_3 = 15 \, \Omega & R_7 = 50 \, \Omega & R_4 = 15 \, \Omega \\
 R_5 = 15 \, \Omega & R_6 = 15 \, \Omega & R_8 = 6 \, \Omega & R_9 = 4 \, \Omega & R_{10} = 10 \, \Omega \\
 R_{11} = 10 \, \Omega & E_2 = 180 \, V & J = 9 \, A & P_{R7} = 0 \, W & 
 \end{array}$$


**Determine:**

- $E_1$ .
- $P_{J1}$ ,  $P_{E2}$ .
- $P_{R8}$ ,  $P_{R9}$ .

Solution:

$$E_1 = 3 \, V, P_{J1} = 3510 \, W, P_{E2} = 270 \, W, P_{R8} = 54 \, W, P_{R9} = 36 \, W$$

## 1.5 DC-05

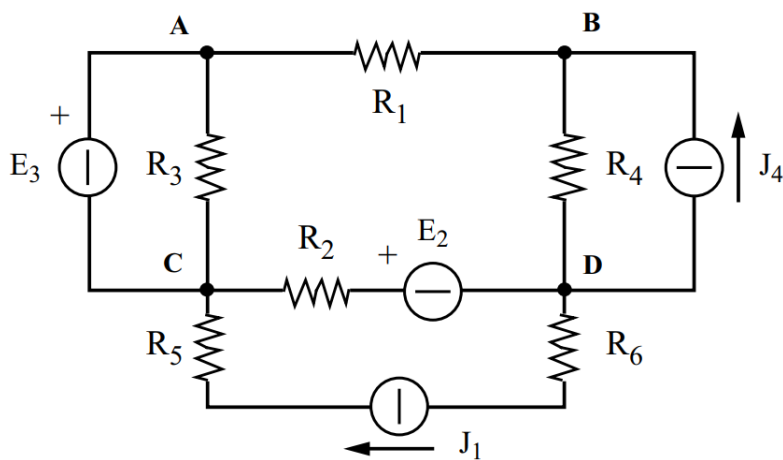

$$\begin{array}{lllll}
 R_1 = 2 \, \Omega & R_2 = 2 \, \Omega & R_3 = 5 \, \Omega & R_4 = 1 \, \Omega & R_5 = 2 \, \Omega \\
 R_6 = 1 \, \Omega & E_3 = 80 \, V & J_1 = 40 \, A & J_4 = 10 \, A & P_{R2} = 0 \, W
 \end{array}$$


**Determine:**

- $P_{R3}$ ,  $P_{R4}$
- $P_{E3}$ ,  $P_{J4}$ .
- $E_2$ .
- $P_{J1}$ .

Solution:

$P_{R3} = 1280 \text{ W}$ ,  $P_{R4} = 2500 \text{ W}$ ,  $P_{E3} = 4480 \text{ W}$ ,  $P_{J4} = 500 \text{ W}$ ,  $E_2 = 50 \text{ V}$ ,  $P_{J1} = 6800 \text{ W}$

## 1.6 DC-06

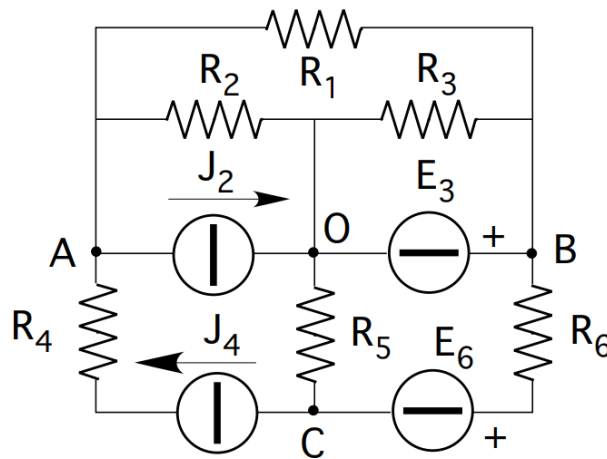

$$\begin{array}{ccccc} R_1 = 20 \, \Omega & R_2 = 30 \, \Omega & R_3 = 30 \, \Omega & R_4 = 30 \, \Omega & R_5 = 20 \, \Omega \\ R_6 = 12 \, \Omega & J_2 = 17.5 \, A & J_4 = 4 \, A & E_3 = 120 \, V & E_6 = -168 \, V \end{array}$$


Assuming  $V_O = 0 \text{ V}$ , **determine:**

- $V_A, V_B, V_C$  potentials.
- $P_{J2}$ ,  $P_{E3}$ ,  $P_{J4}$ ,  $P_{E6}$ .

Solution:

$V_A = -90 \text{ V}$ ,  $V_B = 120 \text{ V}$ ,  $V_C = 150 \text{ V}$ ,  $P_{J2} = 1575 \text{ W}$ ,  $P_{E3} = 3120 \text{ W}$ ,  $P_{J4} = -480 \text{ W}$ ,  $P_{E6} = 1932 \text{ W}$ .

## 1.7 DC-07

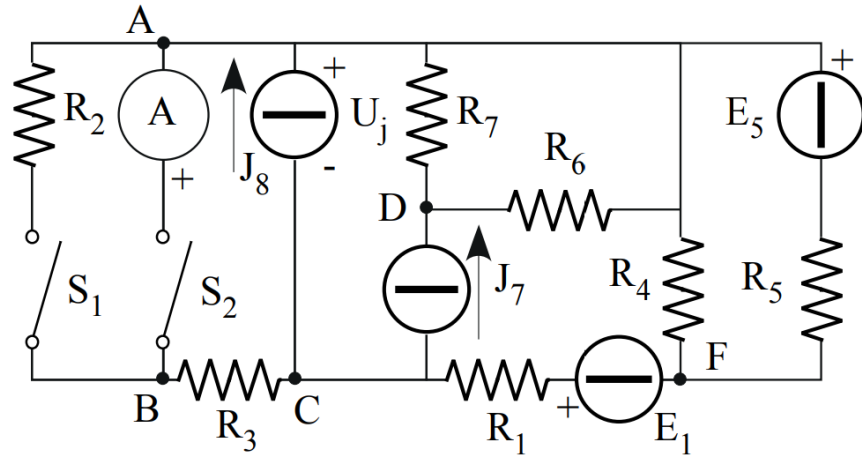

$$I_A = 20 \text{ A} \quad P_{R2} = 5120 \text{ W} \quad R_2 = 20 \Omega \quad R_3 = R_5 = R_1 \quad R_4 = R_6 = R_7 = 2R_1$$


$I_A$  when  $S_1$  open and  $S_2$  close.  $P_{R2}$  when  $S_1$  close and  $S_2$  open, **determine**:

- $R_1$ .
- $U_j$  when both switches are open.
- $P'_{R3}$  and  $U'_j$  when  $S_1$  close and  $S_2$  open.

Solution:

$$R_1 = 30 \Omega, U_j = -1600 \text{ V}, P'_{R3} = 7680 \text{ W}, U'_j = -800 \text{ V}.$$

## 1.8 DC-08

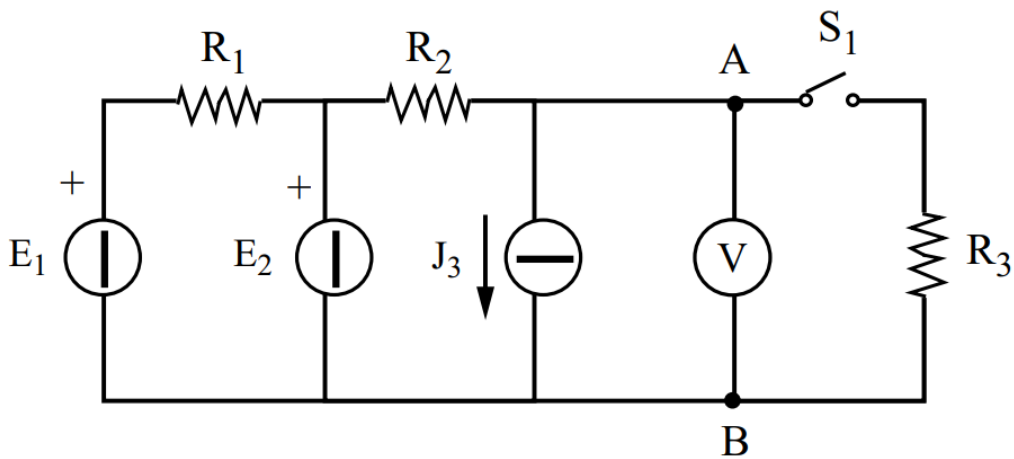

$$\begin{array}{lll} E_1 = 120 \text{ V} & J_3 = 4 \text{ A} & R_1 = 10 \Omega \\ R_2 = 10 \Omega & R_3 = 20 \Omega & U_V = 60 \text{ V} \end{array}$$


$U_V$  measured when  $S_1$  opened. **Determine:**

- $E_2$ .
- $P_{E_1}$ ,  $P_{E_2}$  and  $P_{J_3}$  when  $S_1$  opened.
- $U'_V$  when  $S_1$  closed.
- $P'_{E_1}$ ,  $P'_{E_2}$  and  $P'_{J_3}$  when  $S_1$  closed.

Solution:

$E_2 = 100 \text{ V}$ ,  $P_{E_1} = 240 \text{ W}$ ,  $P_{E_2} = 200 \text{ W}$ ,  $P_{J_3} = -240 \text{ W}$ ,  $U'_V = 40 \text{ V}$ ,  $P'_{E_1} = 240 \text{ W}$ ,  $P'_{E_2} = 400 \text{ W}$ ,  $P'_{J_3} = -160 \text{ W}$ .

### 1.9 DC-09

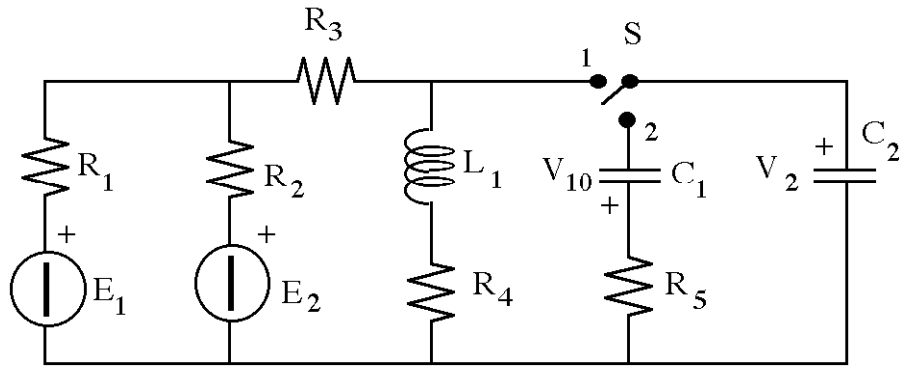

$$\begin{array}{llll} E_1 = 100 \text{ V} & E_2 = 200 \text{ V} & V_{10} = 150 \text{ V} & R_1 = 30 \, \Omega \\ R_2 = 20 \, \Omega & R_3 = 13 \, \Omega & R_4 = 75 \, \Omega & R_5 = 75 \, \Omega \\ L_1 = 0.8 \text{ H} & C_1 = 200 \, \mu\text{F} & C_2 = 100 \, \mu\text{F} & \end{array}$$

The circuit is in steady state when  $S$  is in 1. The capacitor  $C_1$  is charged to voltage  $V_{10}$ . Then the switch is switched to the position 2. **Determine:**

- The energy  $W_0$  stored overall by the circuit.
- The voltage  $V'_2$  at the ends of  $C_1$  when  $S$  is in position 2.
- The electric work  $\mathcal{L}_{R_5}$  absorbed by resistor  $R_5$  when  $S$  switched from 1 to 2.


Solution:

$W_0 = 4.25 \text{ J}$ ,  $V'_2 = -60 \text{ V}$ ,  $\mathcal{L}_{R_5} = 2.43 \text{ J}$ .



## 2 AC CIRCUIT

### 2.1 AC-01

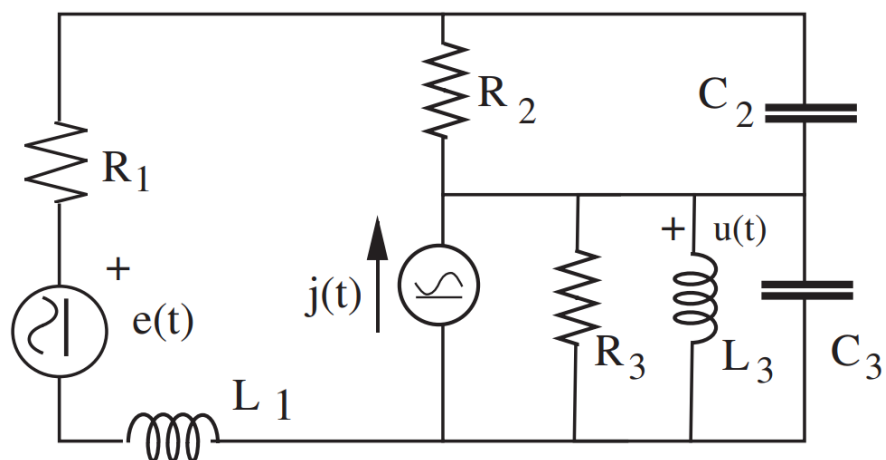

$$\begin{aligned}
 j(t) &= 30 \sin(100t + \frac{\pi}{4}) & e(t) &= 300\sqrt{2} \sin(100t + \frac{\pi}{2}) & R_1 &= R_3 = 10 \, \Omega \\
 R_2 &= 20 \, \Omega & L_1 &= 400 \, mH & L_3 &= 400 \, mH \\
 C_2 &= 500 \, \mu F & C_3 &= 250 \, \mu F
 \end{aligned}$$


**Determine:**

- $u(t)$
- $P_j$  and  $Q_j$
- $P_e$  and  $Q_e$

Solution:

$$\begin{aligned}
 u(t) &= 250\sqrt{2} \sin(100t + 0.9273), \quad P_j = 5250 \, W, \quad Q_j = 750 \, var, \quad P_e = 1500 \, W \\
 Q_e &= 3.3448 \cdot 10^{-13} \, var
 \end{aligned}$$

### 2.2 AC-02

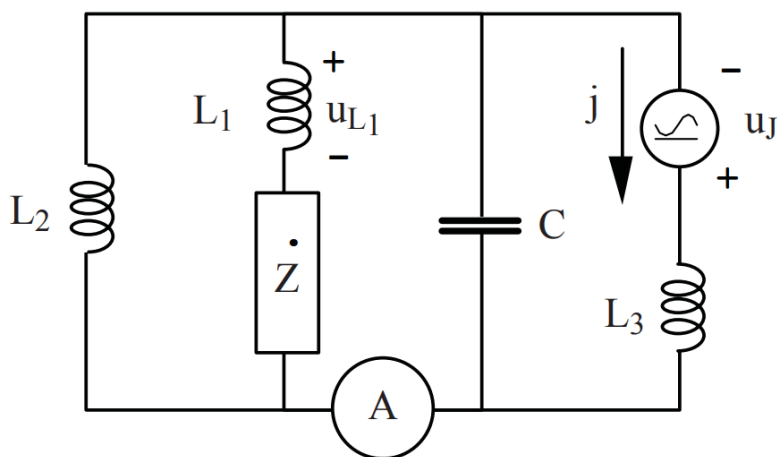

$$L_1 = 10 \text{ mH} \quad L_2 = 15 \text{ mH} \quad L_3 = 15 \text{ mH} \quad C = 25 \text{ } \mu\text{F}$$

$$u_{L_1}(t) = 320 \cdot \sin(1000t + \frac{\pi}{4}) \quad I_A = 0 \text{ A}$$

**Determine:**


- $\dot{Z} = R + jX$
- $Q_{L_2}$
- $j(t)$  and  $u_j(t)$
- $Q_{L_3}$

Solution:

$$\dot{Z} = -25j, \quad Q_{L_2} = 7680 \text{ var}, \quad j(t) = 12 \cdot \sin(1000t + \frac{3}{4}\pi), \quad u_j(t) = 300 \cdot \sin(1000t + \frac{\pi}{4}),$$

$$Q_{L_3} = 1080 \text{ var}$$

### 2.3 AC-03

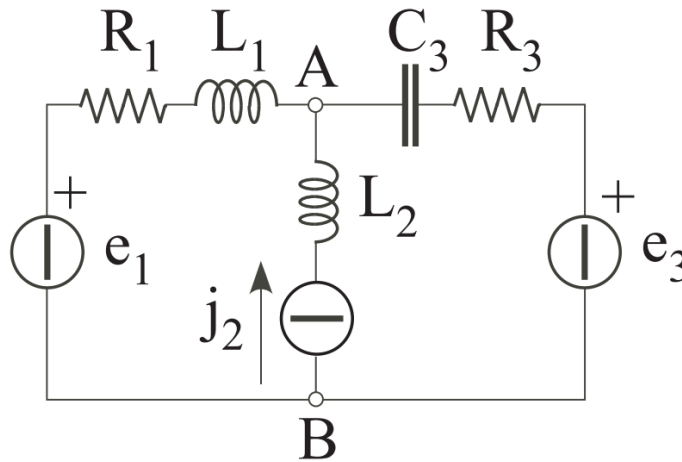

$$e_1(t) = 100 \sin(1000t) \quad j_2(t) = 8 \cos(1000t) \quad e_3(t) = 200 \sin(1000t)$$

$$R_1 = 5 \text{ } \Omega \quad R_3 = 10 \text{ } \Omega \quad L_1 = 5 \text{ mH}$$

$$L_2 = 10 \text{ mH} \quad C_3 = 100 \text{ } \mu\text{F}$$

**Determine:**


- $P_{R_1}$  and  $P_{R_3}$
- $P_{E_1}$ ,  $P_{J_2}$  and  $P_{E_3}$
- $S_{J_2}$
- $i_{e_3}(t)$

Solution:

$$P_{R_1} = 776 \text{ W}, \quad P_{R_3} = 848 \text{ W}, \quad P_{E_1} = -920 \text{ W}, \quad P_{J_2} = 704 \text{ W}, \quad P_{E_3} = 1840 \text{ W}, \quad S_{J_2} = 729.71 \text{ VA},$$

$$i_{e_3}(t) = 13.023 \sin(1000t + 0.043451)$$

## 2.4 AC-04

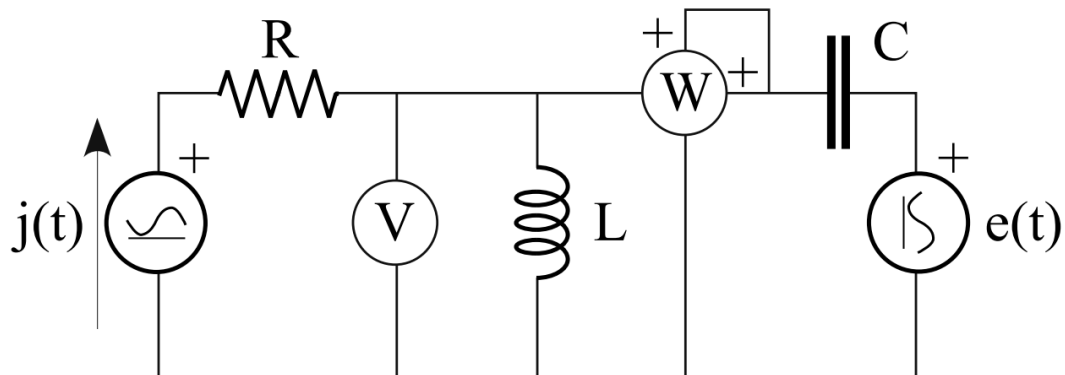

$$e(t) = 100 \cdot \sqrt{2} \sin(200t) \quad j(t) = 10 \cdot \sqrt{2} \sin(200t + \pi) \quad R = 5 \, \Omega$$

$$L = 100 \, \text{mH} \quad C = 500 \, \mu\text{F}$$

**Determine:**

- The indication of the voltmeter  $U_V$
- $P_W$
- $u_j(t)$
- $i_e(t)$
- $P_j$  and  $Q_j$

Solution:

$$U_V = 282.84 \, \text{V}, \quad P_W = 2000 \, \text{W}, \quad u_j(t) = 353.55 \cdot \sin(200t + 0.9273), \quad i_e(t) = 31.623 \cdot \sin(200t - 0.46365)$$

$$P_j = -1500 \, \text{W}, \quad Q_j = -2000 \, \text{var}$$